

Download Datasheet

Texas Instruments

EEVblog Elect	ronics Community Forum			
	A Free & Open Forum For Electronics Enthusiasts & Professionals			
Hello JimBeam Show unread posts since la Show new replies to your p November 29, 2015, 05:03	posts.			
🏠 Home 🔞 Help 🔍	Search 🧟 Profile About us 🖂 My Messages 🛗 Calendar Links 趮 Members 🤤 Logout			
EEVblog Electronics Commu	nity Forum » Electronics » Projects, Designs, and Technical Stuff » Rigol DG1022 improvement thread			
Pages: [1] Go Down	REPLY NOTIFY MARK UNREAD SEND THIS TOPIC PRINT SEARCH			
Author	Topic: Rigol DG1022 improvement thread (Read 1195 times)			
0 Members and 0 Guests are	e viewing this topic.			
c4757p Super Contributor	Rigol DG1022 improvement thread « on: August 18, 2014, 08:09:36 AM »			
	Two separate 'repair'/awful design correction attempts in this thread.			
Posts: 7514 Country: 🛀 Arrow Q	The DG1022 has a pretty noisy output. All the noise is above the bandwidth, making it pretty easy to remove with an LPF - though the bands are <i>close</i> (within less than half a decade), requiring a good, precise filter. I've designed and tested a nice, inline output filter for it, seventh order Bessel with integrated common-mode filter, which puts the output noise down within the noise floor of my scope. I'll post more on that later - PCBs, BOM, plus I have a couple extras (first come, first served).			
	However, while I was characterizing it, I had to push something else onto my stack:			
	My Rigol DG1022U does this sometimes:			
	Tek Stop: 2GS/s 143 Acqs			



But sometimes, it even does *this*:



The cause appears to be related to this, er, *special* output amplifier layout:



I've confirmed that another unit does the first one, but not the second. A bit more later tonight on an attempt to fix it. Has anybody else seen output amplifier instability like this?





wtfrigol.jpg (276.87 kB, 808x606 - viewed 503 times.)

« Last Edit: August 18, 2014, 08:18:03 AM by c4757p »

Report to moderator 🏼 Hogged

Quote

c4757p

Super Contributor



Posts: 7514

Country: 💻 🎴 🖂 🧔 Re: Rigol DG1022 improvement thread « Reply #1 on: August 18, 2014, 09:54:30 AM »

Bodge time! Look at this hideous atrocity. This is what happens when I attempt PCB modification on a board that's still mounted in chassis.



Fixed, though. Here's the worst I can get (which matches with another, better behaved unit):





Report to moderator Logged

"" Quote

c4757p

Super Contributor



Country: 🔤

💄 🖂 🖗

Re: Rigol DG1022 improvement thread « Reply #2 on: August 18, 2014, 10:40:23 AM »

Now that my DG1022 is repaired to what most DG1022s should be, (void)stack_pop(&dg1022);

If you want to improve the output noise performance, there are two things you can do. The first is simple: Rigol uses *terrible* cables to run from the main board to the front panel jacks. They pick up a *ton* of common-mode and normal-mode garbage.

Unfortunately, I don't have a picture of my DG1022's output before replacing the cables. Already tossed out my old ones, and anyway, these have quite fragile connectors and I don't want to go plugging and unplugging them. I may have some to append to this thread in a while though; I know someone who, I think, has some spec-an shots of the same thing.

Tek Stop: Single Seq 1GS/s T-I Ch1 RMS 302.1µV 1⊇ ,

Here is the noise floor of my oscilloscope, for comparison:



Here's the DC output of the DG1022 with the cable replaced. Probably, anyone who has an unmodified DG1022 can verify that it's normally much worse:



This one's easy: you just need a couple cables that aren't made of shit. <u>TE Connectivity 2015357-3</u> is what I used. Be careful when replacing them - the gunk they stuck the original ones down with is very strong, and you could rip the sockets right off the PCB if you pull it off roughly.



That's not all, though. Certain output modes cause significantly more output noise to be generated. You can see that in my second post. It's not much, but it *is* a good 5mVpp, which is *way* too much for an



c4757p

Super Contributor

Posts: 7514 Country: 🔤 A 🖸 🖓 instrument that should be able to do 2mVpp output signal. When your SNR is less than unity, you can hardly call it a signal generator anymore, can you?

Adding an inline filter directly before the output connector corrects Rigol's poor filter design, bringing the output back under my scope's noise floor:



The nature of the noise requires a nice, sharp cutoff right after the function generator's bandwidth, because the bandwidth is 25 MHz and the noise starts at 70 MHz. The filter has to be close to flat at 25 MHz, and then "fully attenuated" half a decade later. This calls for a relatively high-order Bessel filter:



Excuse the lack of a proper model to hold the equivalent circuit for the common-mode chokes!

This filter works to bring every nasty bit of the DG1022's output under my scope's noise floor - good enough for me!

PCBs, schematic, BOM shortly. I have two spare PCBs (plus one already called for), which I'll give away free to anyone to whom I can send it for the price of a postage stamp. I'll share the project on OSH Park as well, so everyone else can have one for \$just_above_nothing.



dc_fft_0v6.png (3.45 kB, 640x480 - viewed 49 times.)

DavidH

🚨 📿



Yes - except the output was *flat* for all of these. This is the DC "waveform" 🥝





Posts: 7514 Country: 🔜

c4757p

Super Contributor



Posts: 7514 Country: 🔤

Pages: [1] Go Up

Re: Rigol DG1022 improvement thread « Reply #8 on: August 18, 2014, 12:32:13 PM »

Cuote

Okay, here's the stuff.

An almost completely assembled board. You can see that this is fiddly - not for the faint of heart. The dual ferrites are particularly irritating to solder - I recommend reflow if available. Also pay attention to the orientation of these.



Gerbers are in gerbers.zip and can be sent off to damn near anyone. The KiCad project is in proj.zip, and there's a PDF of the schematic attached as well. The BOM can be imported by DigiKey's BOM importer.

There are still two boards left, so PM me if you want one. Beyond that, order them for about \$9 from OSH Park, here

To connect it, simply use the replacement cables (get rid of the awful Rigol ones...) to connect the filters inline with each of the two channels. Mounting is tricky - I just stuck it to the case with tape

Edit: Updated BOM to include manufacturer part numbers

Note: The BOM as it is contains the exact number of the parts you need. However, if you drop one on the floor, you'll never see it again. (Guess why there's a part missing in my example photo.....) I highly recommend buying more of the inductors and capacitors than you need.





Jump to: => Projects, Designs, and Technical Stuff 🗘 go

EEVblog Electronics Community Forum » Electronics » Projects, Designs, and Technical Stuff » Rigol DG1022 improvement thread

LINK TO CALENDAR

EEVblog Main Site	EEVblog on Youtube	EEVblog on Twitter	EEVblog on Facebook		
SMF 2.0.11 SMF © 2015, Simple Machines					

5MF 2.0.11 | SMF © 2015, Simple Machine Simple Audio Video Embedder SMFAds for Free Forums XHTML RSS Mobile WAP2